

FSM 2 : Finite State Machines

Ask Week 8 Questions here...

You can ask questions during the week using slido here :

<https://app.sli.do/event/ctKC3fn54pdrvZE1sQLLok7>

Or at slido.com + **#ee202604**

Or the tiny little QR :



Let's Try This Out...



Bob is stressed out as he has too many deadlines and isn't sleeping enough! He has decided to develop a FSM to regulate his time between sleeping and studying.

- When he is idle, there are two actions he can do next : SLEEP or STUDY.
- To prevent exhaustion, he buys a body exhaustion sensor and checks it every hour. When he is exhausted, the sensor output EX will be TRUE.
- When he is exhausted, he should sleep (SLEEP is TRUE). When he is not exhausted, he should study (STUDY is TRUE).
- Implement his FSM using D Flip Flops and gates.




Step 1 : Block Diagram, STD

1) Block Diagram




2) State Transition Diagram

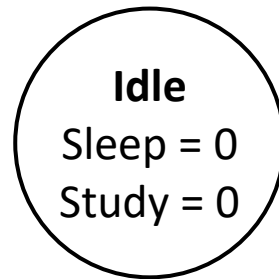

Step 2 : Next State Table

State Transition Diagram

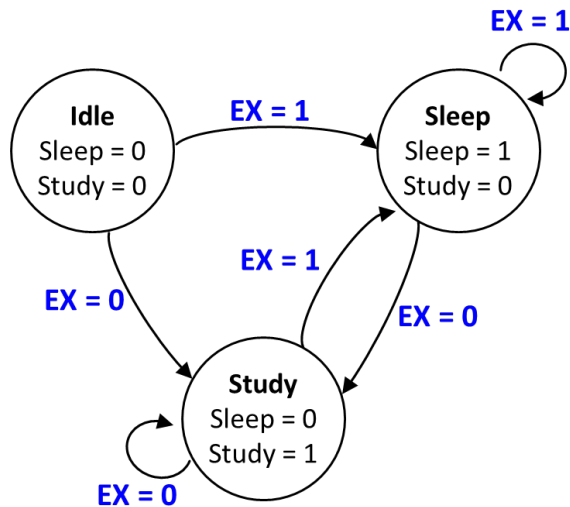

Current State Input Next State

S		S+

S_1S_0	EX	S_1+S_0+

State	S_1S_0
	00
	01
	10

Step 2 : Next State Table

S_1S_0	EX	$S_1^+S_0^+$
0 0	0	1 0
0 0	1	0 1
0 1	0	1 0
0 1	1	0 1
1 0	0	1 0
1 0	1	0 1

$D_1 =$

$D_0 =$

$D_1:$

S_1S_0	00	01	11	10
EX				
0				
1				

$$S_1^+ = \overline{EX}$$

$D_0:$


S_1S_0	00	01	11	10
EX				
0				
1				

$$S_0^+ = EX$$




Step 2 : Next State Table

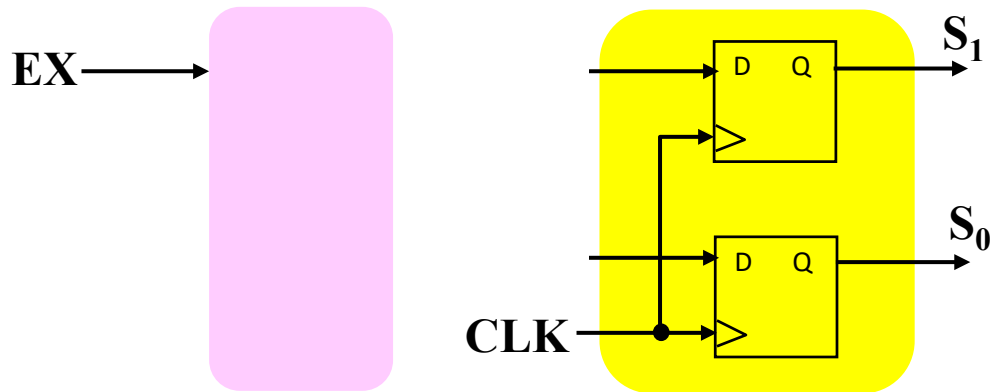If the state assignments were to change, would the next state logic change?



Step 3 : Output Logic


State	S_1S_0
IDLE	00
SLEEP	01
STUDY	10

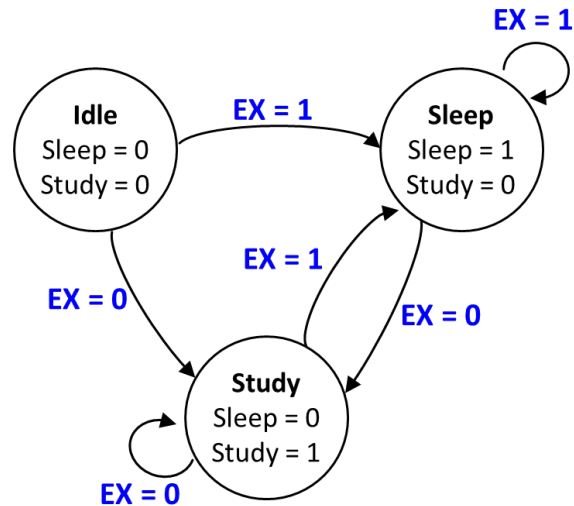

S_1S_0	Sleep	Study
0 0		
0 1		
1 0		


Sleep =

Study =

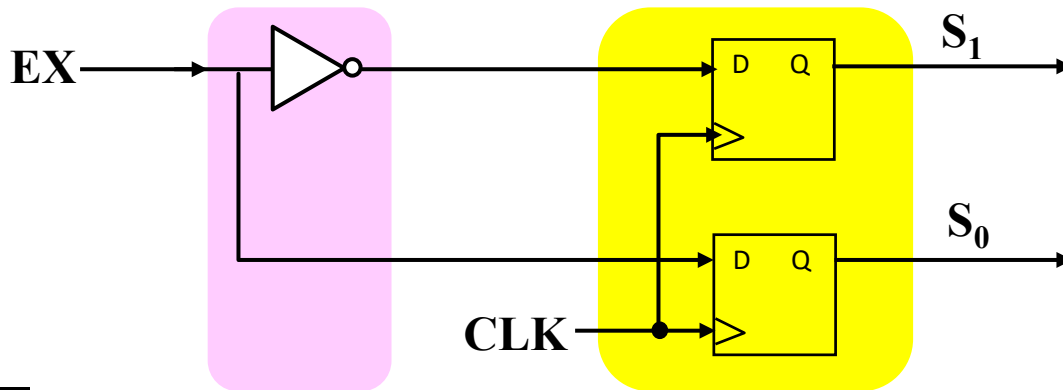

Step 3 : Output Logic


State	S_1S_0
IDLE	00
SLEEP	01
STUDY	10

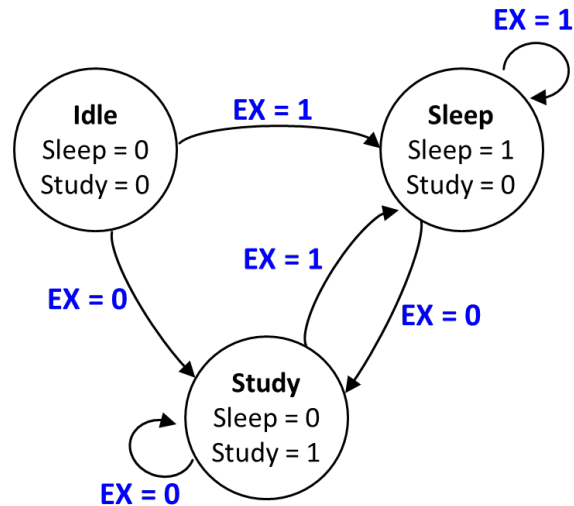

S_1S_0	Sleep	Study
0 0	0	0
0 1	1	0
1 0	0	1

$$\begin{aligned}\text{Sleep} &= \overline{S_1}S_0 \\ &= S_0\end{aligned}$$
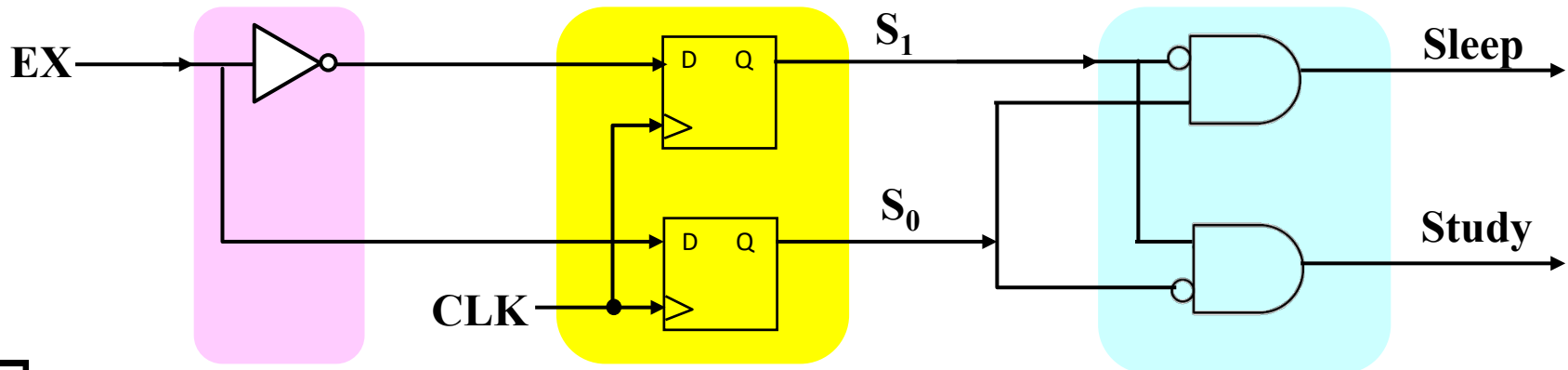
$$\begin{aligned}\text{Study} &= S_1\overline{S_0} \\ &= S_1\end{aligned}$$




Changing Sleep Time...




Bob has decided that he is sleep state for too long and has decided to fix his sleep time to 5 hours.

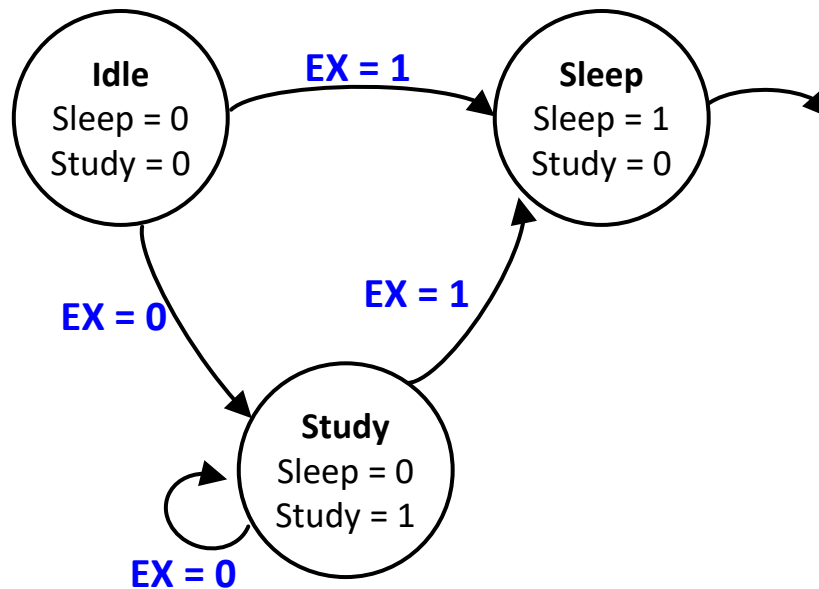How can we modify his state transition diagram?




Modular Design of FSMs

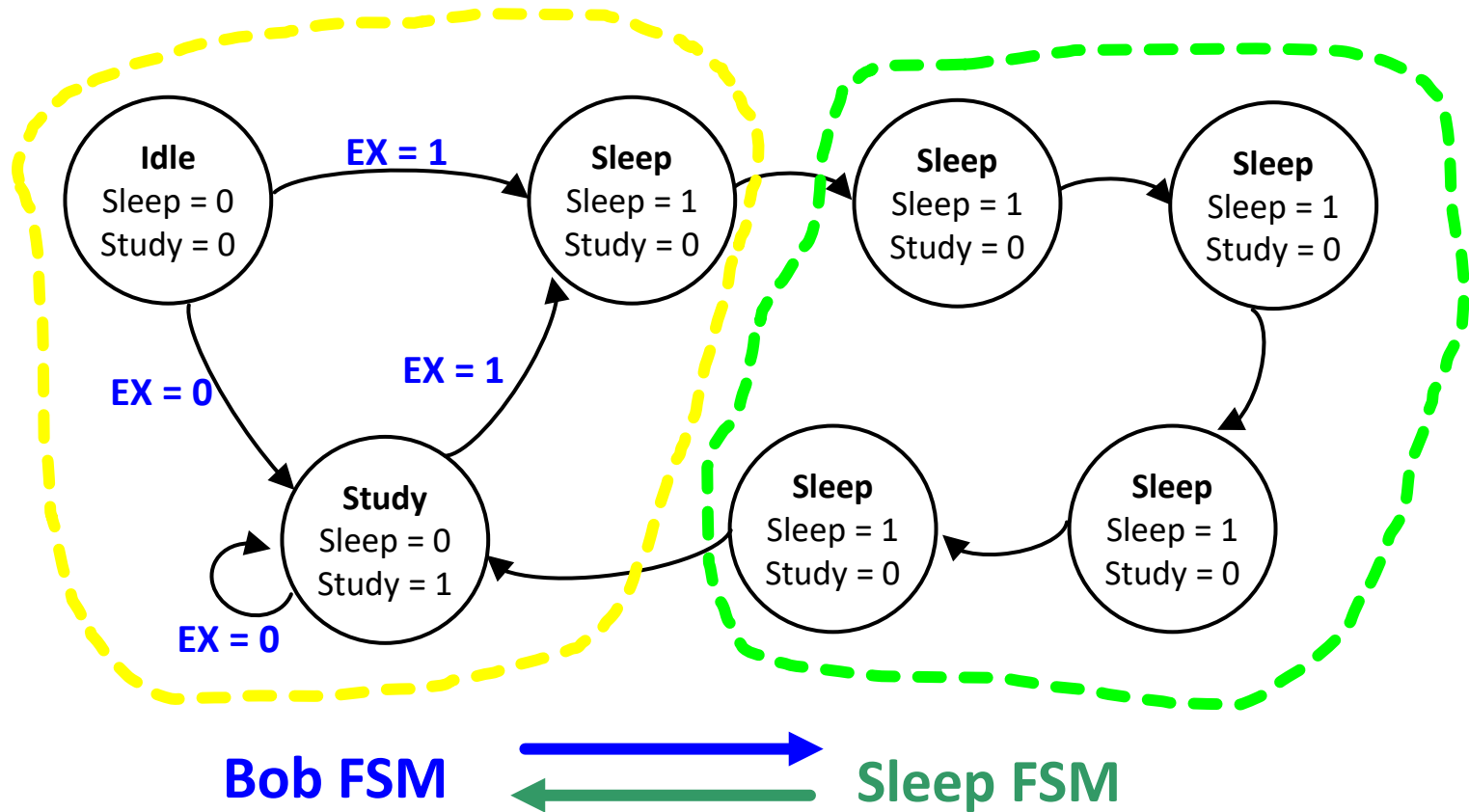Designing complex FSMs is often easier if they can be broken down into simpler FSMs that interact.




Modular Design of State Machines

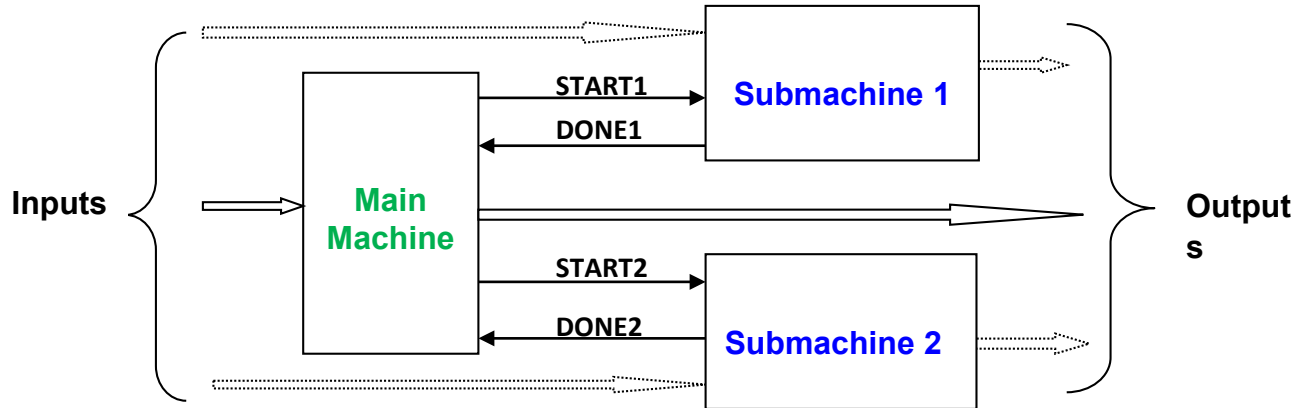


- **Main machine** : executes main algorithm, controls the **submachines** & get the job done. Commands & gets feedback signals from **submachines**.
- **Submachines** respond to external inputs & commands from **main machine**. Can give outputs as well as feedback to the **main machine**.
- Common examples of **submachines** are **counters**, **shift registers**, etc.
- Sometimes the **main machine** is called the **controller** and the **submachines** are called **controlled circuit elements** or **architectural elements**.
- **Trick here** is to **modularize** appropriately, and pick suitable components for the submachines that simplify the design problem.

Modularizing...

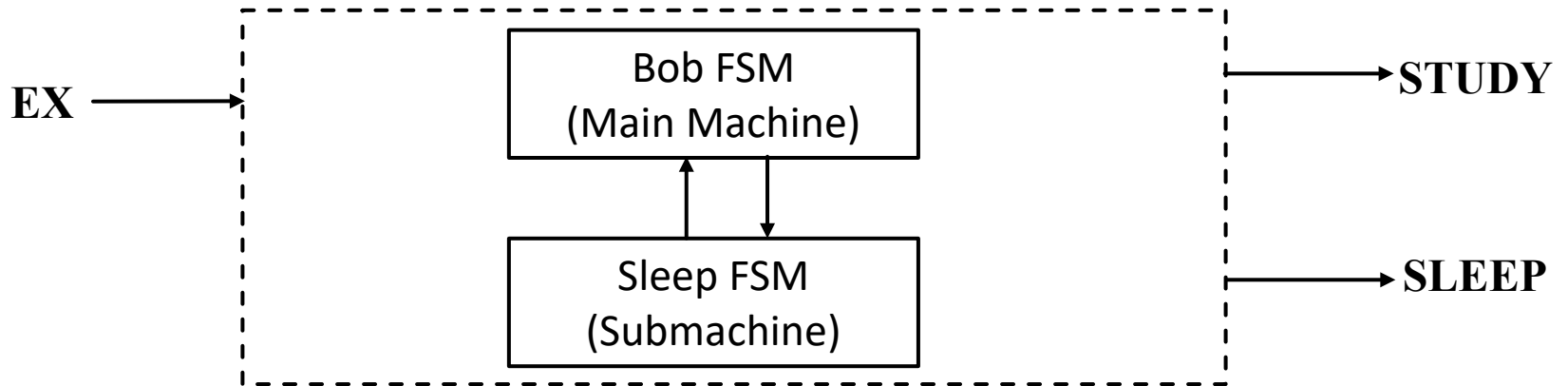
What is a natural submachine that we can use?



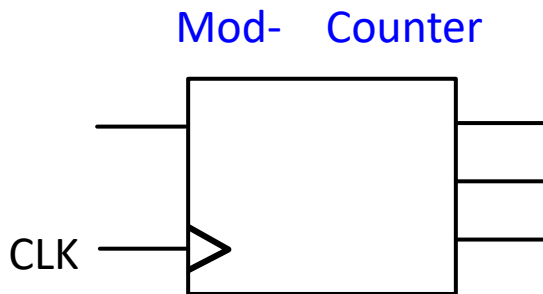
What inputs would you provide? What outputs would you want?



FSM with Architectural Element

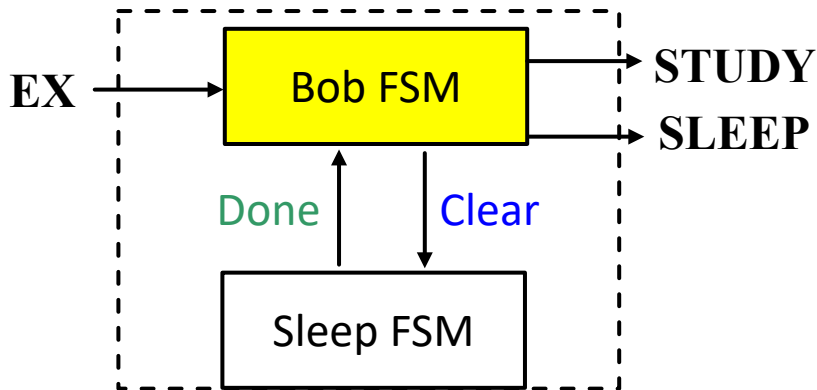


Sleep FSM


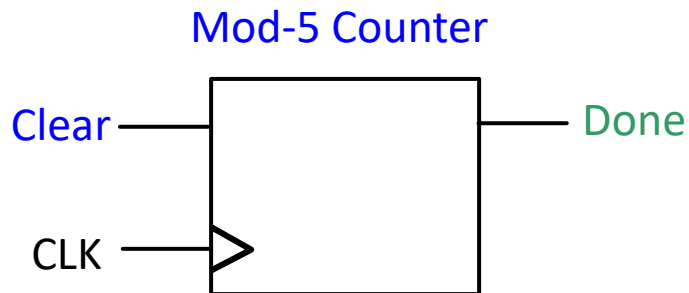


Done = 1 when count = 4 (100)

Bob FSM

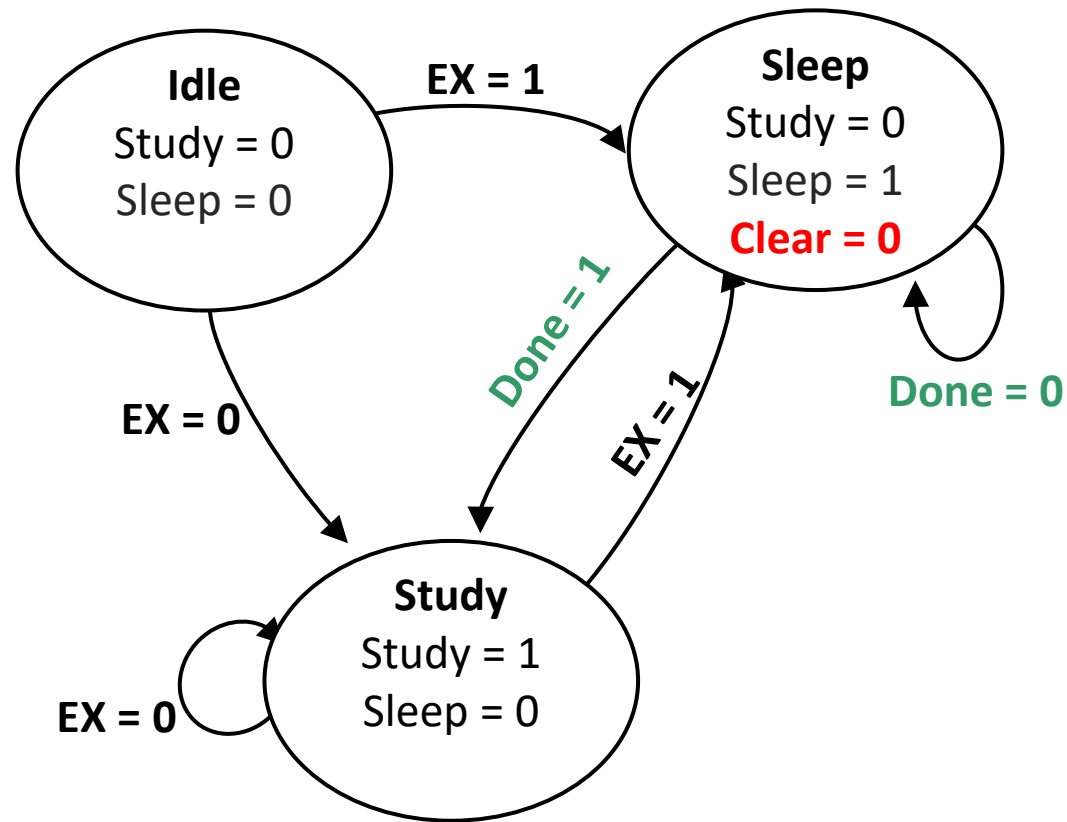

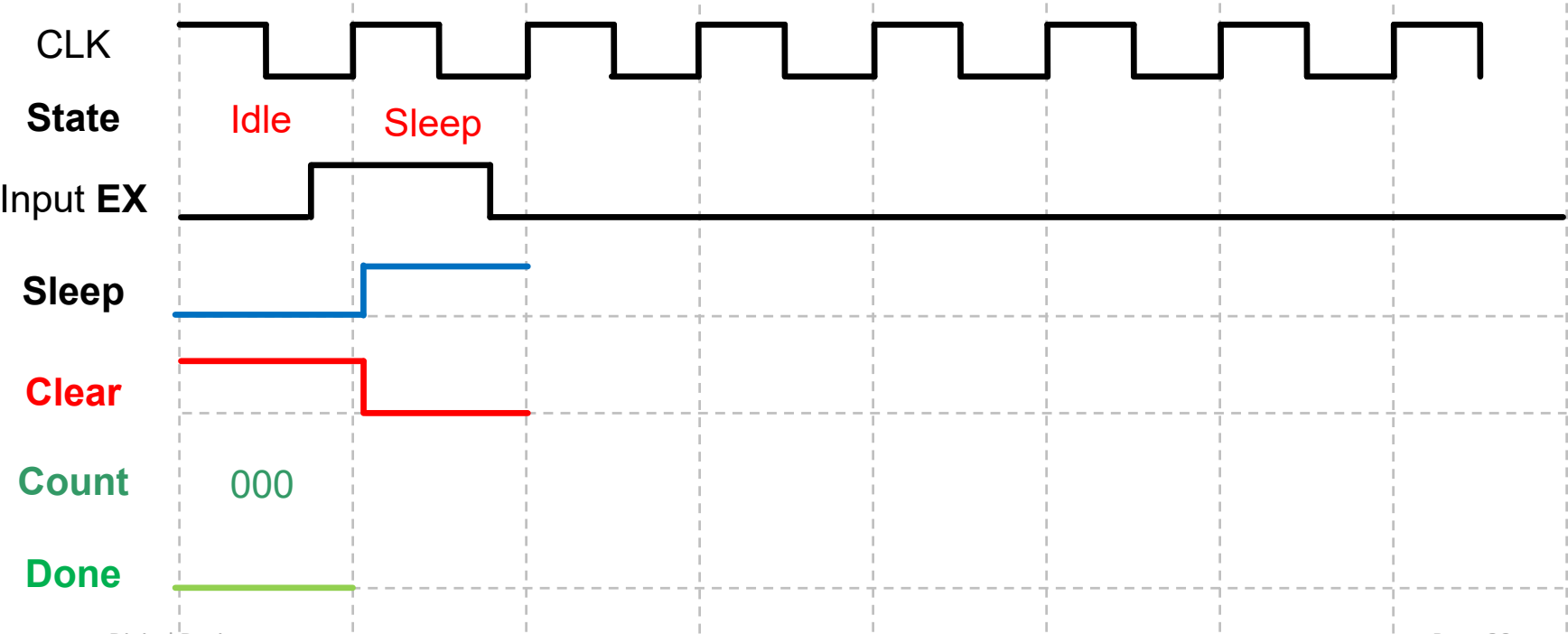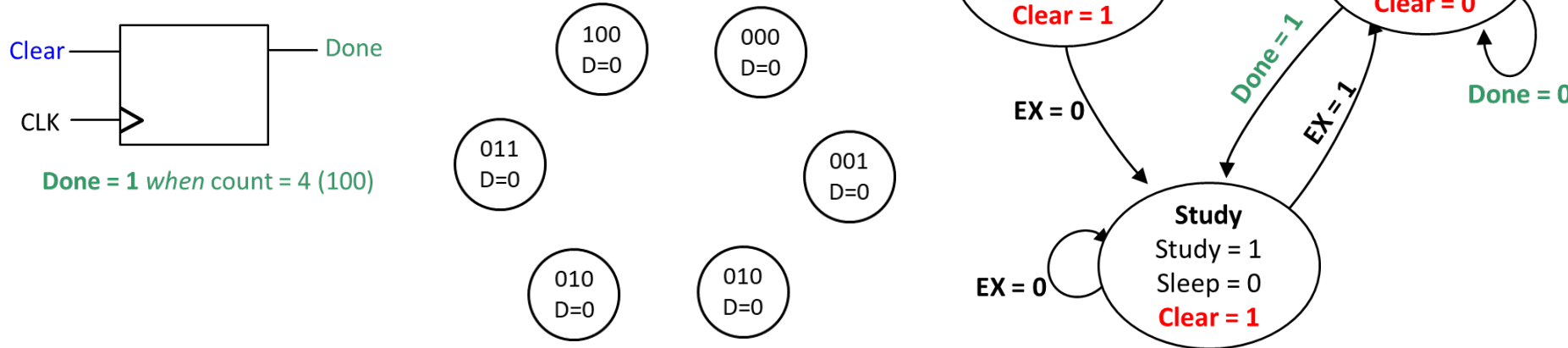Fill in the timing diagram for Bob
FSM and the counter.



Fill in the timing diagram for Bob
FSM and the counter.

