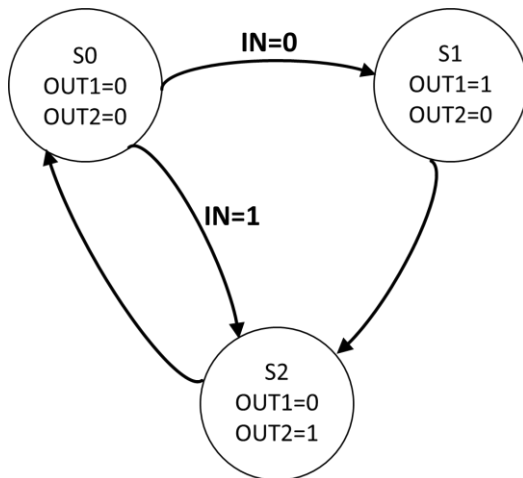


Tutorial 10 (SOLUTIONS)

NOTE THAT THERE ARE MANY OTHER POSSIBLE SOLUTIONS TOO...

SS1

1) State Transition Diagram



2) Next State Table

Current State	Inputs	Next State
S	IN	S+
S0	0	S1
S0	1	S2
S1	X	S2
S2	X	S0

By using two bits to represent the state, S_1S_0 :

State Assignment	S_1	S_0
S0	0	0
S1	0	1
S2	1	0
S3	1	1



Current State		Inputs	Next State	
S ₁	S ₀	IN	S ₁ +	S ₀ +
0	0	0	0	1
0	0	1	1	0
0	1	X	1	0
1	0	X	0	0
1	1	X	0	0

The next state after S3 has been set to S0 instead of don't cares. This is a minimum-risk design choice because there is no external reset signal to this FSM.

A two bit counter can be designed using D Flip-flops for the state memory :

S_1S_0	IN	
	0	1
00	0	1
01	1	1
11	0	0
10	0	0

S_1S_0	IN	
	0	1
00	1	0
01	0	0
11	0	0
10	0	0

$$D_1 = S_1^+ = \overline{S_1} IN + \overline{S_1} S_0 \quad D_0 = S_0^+ = \overline{IN} \overline{S_1} \overline{S_0}$$

3) Output Logic Table


Current State	Outputs	
S	OUT1	OUT2
S0	0	0
S1	1	0
S2	0	1



Current State		Outputs	
S₁	S₀	OUT1	OUT2
0	0	0	0
0	1	1	0
1	0	0	1
1	1	X	X


$$OUT_1 = S_1 = \overline{Q_1}Q_0, \quad OUT_2 = S_2 = Q_1\overline{Q_0}$$

4) Circuit Implementation

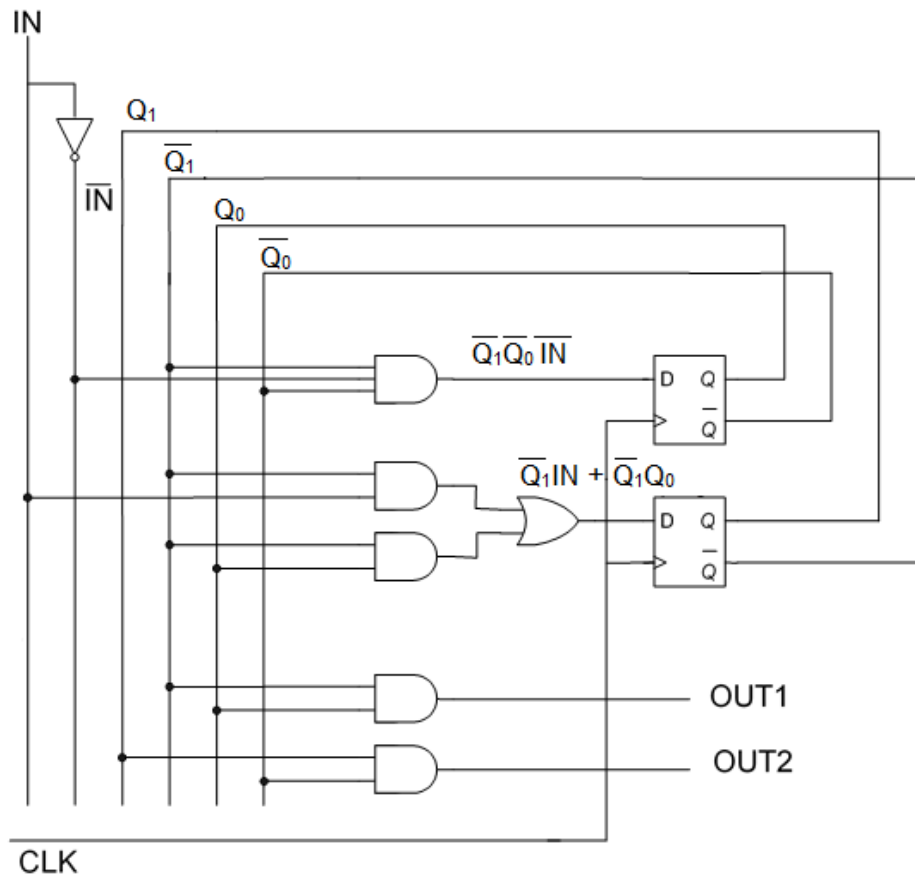

Notice that this is a Moore machine as the outputs (OUT1, OUT2) are a function of the current state (Q_1, Q_0) only.

1) State Transition Diagram

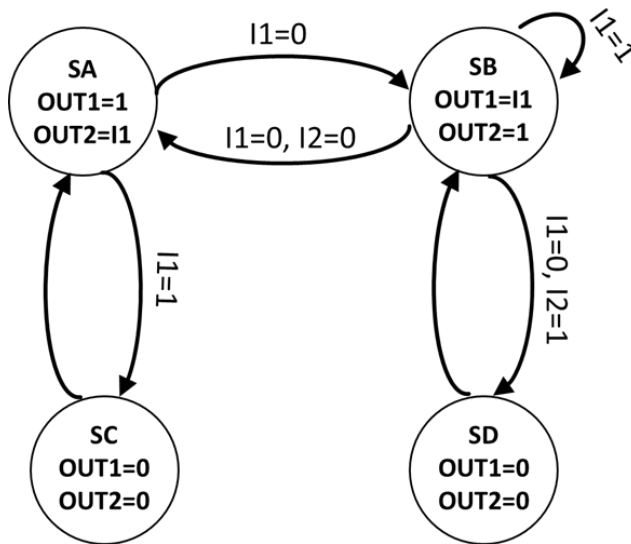

2) Next State Table

Current State	Inputs		Next State
S	I1	I2	S+
SA	0	X	SB
SA	1	X	SC
SB	0	0	SA
SB	0	1	SD
SB	1	X	SB
SC	X	X	SA
SD	X	X	SB

You can arrange the next state table like a KMAP to save yourself one step!

	I ₁ , I ₂			
	00	01	11	10
SA	SB	SB	SC	SC
SB	SA	SD	SB	SB
SD	SB	SB	SB	SB
SC	SA	SA	SA	SA

A two bit counter can be designed using D Flip-flops for the state memory.

Applying the following State Assignment

	Q ₁	Q ₀
SA	0	0
SB	0	1
SC	1	0
SD	1	1

		I ₁ I ₂			
		00	01	11	10
Q ₁ Q ₀	00	0	0	1	1
	01	0	1	0	0
	11	0	0	0	0
	10	0	0	0	0

		I ₁ I ₂			
		00	01	11	10
Q ₁ Q ₀	00	1	1	0	0
	01	0	1	1	1
	11	1	1	1	1
	10	0	0	0	0

$$D_1 = Q_1^+ = \overline{Q_1} \overline{Q_0} I_1 + \overline{Q_1} Q_0 \overline{I_1} I_2$$

$$D_0 = Q_0^+ = \overline{Q_1} \overline{Q_0} \overline{I_1} + Q_1 Q_0 + Q_0 I_2 + Q_0 I_1$$

3) Output Logic Table


Current State	Outputs	
S	OUT1	OUT2
SA	1	I1
SB	I1	1
SC	0	0
SD	0	0

By inspection,

$$\begin{aligned}
 OUT1 &= SA + SB.I_1 \\
 &= \overline{Q_1}\overline{Q_0} + \overline{Q_1}Q_0I_1 = \overline{Q_1}\overline{Q_0} + \overline{Q_1}I_1
 \end{aligned}$$

$$\begin{aligned}
 OUT2 &= SB + SA.I_1 \\
 &= \overline{Q_1}\overline{Q_0}I_1 + \overline{Q_1}Q_0 = \overline{Q_1}Q_0 + \overline{Q_1}I_1
 \end{aligned}$$

4) Circuit Implementation

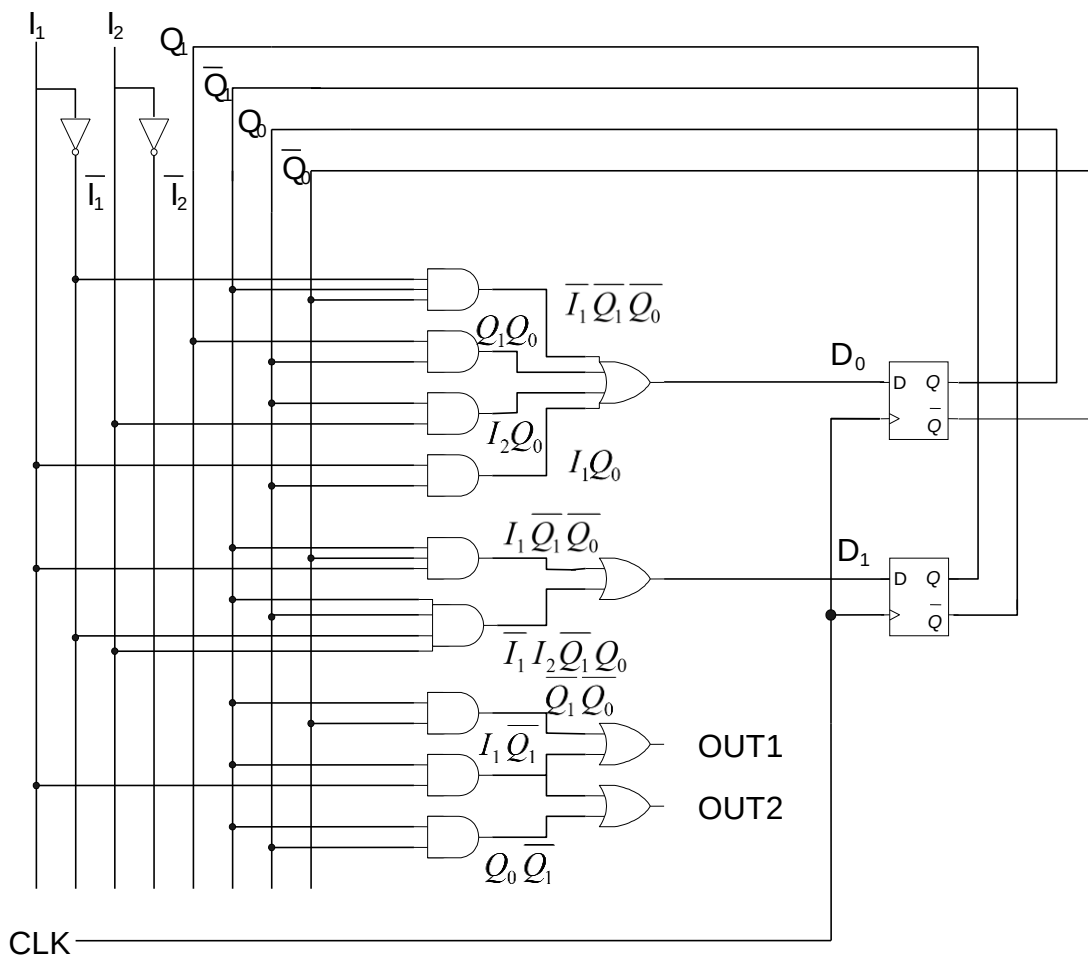


As the outputs, $OUT1$ and $OUT2$, are a function of both current state (Q_1 , Q_0) as well as the current inputs (I_1 , I_2), this is a Mealy machine.

Question 1


Selecting a clock period of 10 seconds, the snooze can be implemented by having 1 state of alarm (10 seconds) followed by 6 states of waiting (60 seconds).

Solution 1 :

Overall Block Diagram:

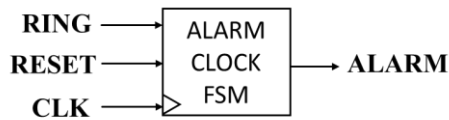


Alarm Clock FSM :

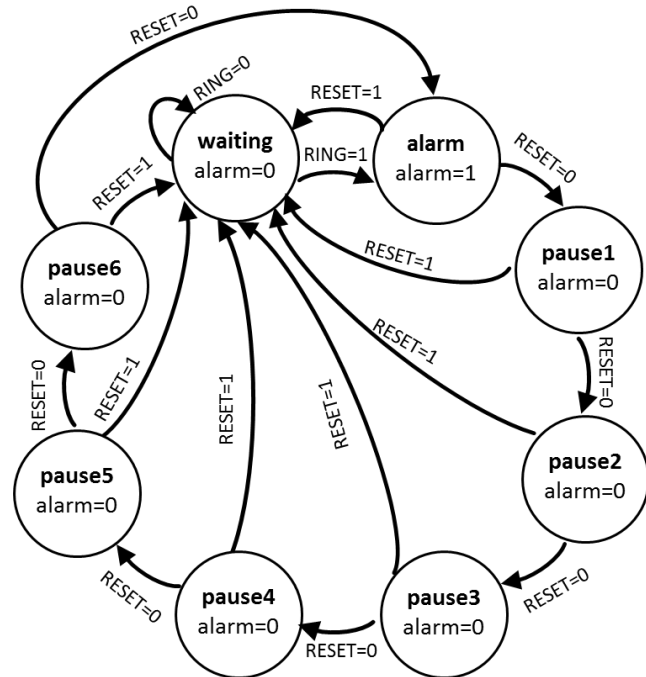


Solution 2 :


Modular FSM Block Diagram:

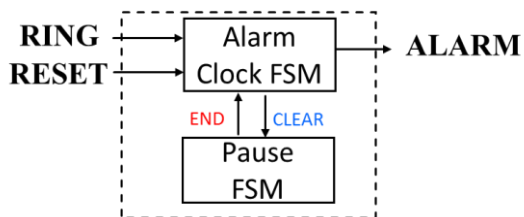

Alarm Clock FSM

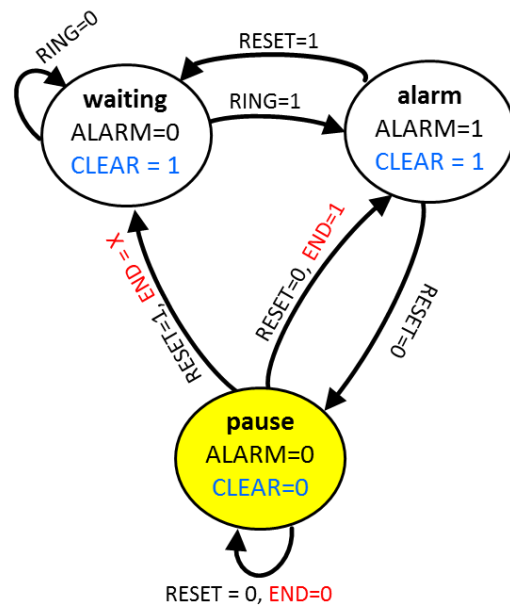


Pause FSM


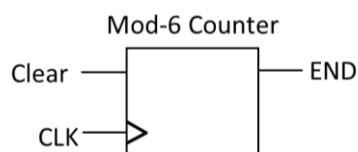


END= 1 when count = 5 (101)

Question 2

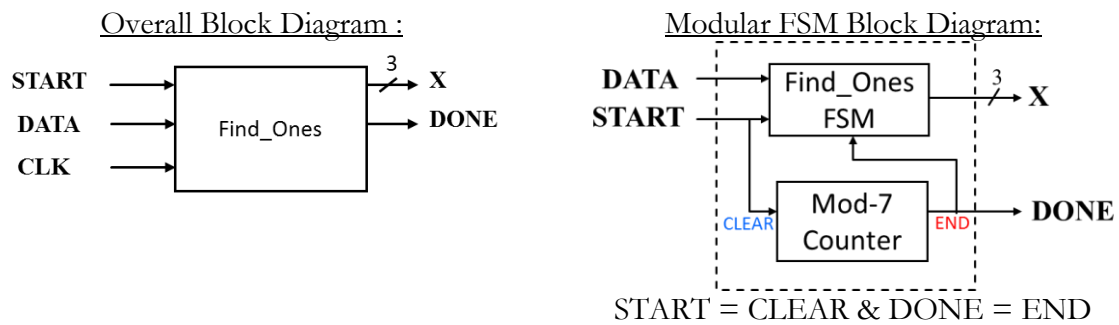

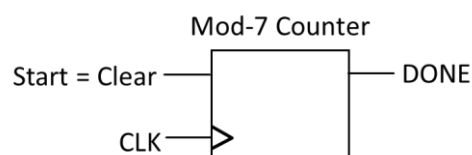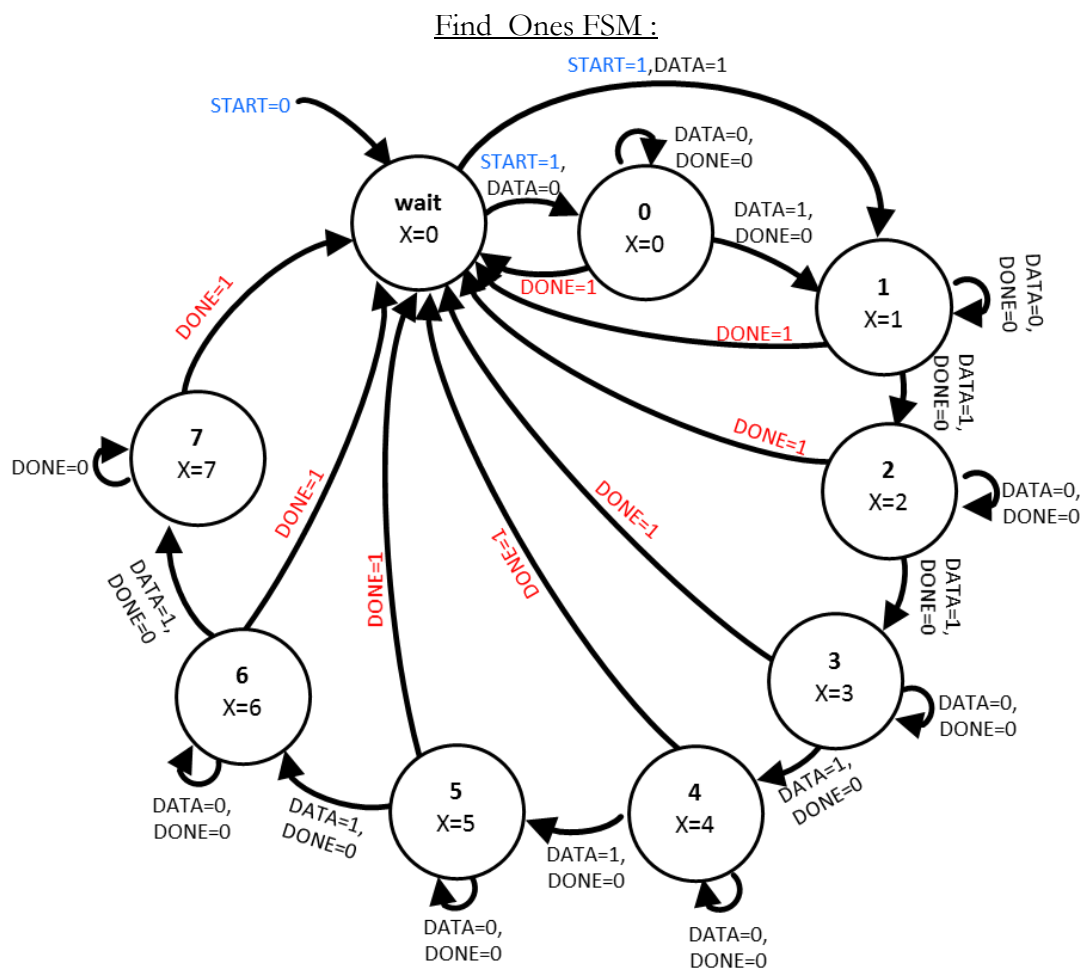By reusing the START signal as the CLEAR signal, and the DONE signal as the END signal, we save two signals.



DONE= 1 when count = 6 (110)

Question 3

Overall Block Diagram :



State Transition Diagram of PPL_COUNTER FSM :

