

EE2026

Digital Design

LOGIC GATES

Massimo ALIOTO

Dept of Electrical and Computer Engineering

Email: massimo.alioto@nus.edu.sg

Get to know the latest silicon system breakthroughs from our labs in 1-minute video demos





Outline


- Logic gate introduction
 - AND/NAND, OR/NOR, NOT/buffer, XOR/XNOR
- Levels of abstraction: Boolean function, truth table, graphical, Verilog
- Implementation of Boolean function using gates
- Design simplification via algebraic manipulations
- Positive and negative logic
- Implementation of Boolean function with gate-level netlist

Introduction to Logic Gates

- Logic gates are digital circuits implementing fundamental Boolean operators or some simple combination of them
 - Abstraction: actually made up of transistors (not shown here), closer to physical implementation of digital systems

  logic gate	symbol	function (F)	logic gate	symbol	function (F)
AND		$A \cdot B$	NAND		$\overline{A \cdot B}$
OR		$A + B$	NOR		$\overline{A + B}$
NOT		$\bar{A}$	Buffer		A

AND and NAND Gates

 

Truth table (AND, NAND)

A	B	$A \cdot B$	$\overline{A \cdot B}$
0	0	0	1
1	0	0	1
0	1	0	1
1	1	1	0

AND

- F is 1 only when both A and B are 1



```
module andgate(A, B, F);  
  input A, B;  
  output F;  
  assign F = A & B;  
endmodule
```

NAND

- F is 0 only if both A and B are 1

```
module nandgate(A, B, F);  
  input A, B;  
  output F;  
  assign F = ~(A & B);  
endmodule
```

OR and NOR Gates

  

OR

- F is 1 when either A or B are 1

```
module orgate(A, B, F);  
  input A, B;  
  output F;  
  assign F = A | B;  
endmodule
```

Truth table (OR, NOR)

A	B	$A + B$	$\overline{A + B}$
0	0	0	1
1	0	1	0
0	1	1	0
1	1	1	0




NOR

- F is 1 only if both A and B are 0

```
module norgate(A, B, F);  
  input A, B;  
  output F;  
  assign F = ~(A | B);  
endmodule
```

XOR and XNOR Gates

   - Logic gate that is not fundamental in Boolean algebra
 - But very useful (e.g., arithmetic circuits – see week 4)



XOR

bubble = complement

- F is 1 when either A or B (exclusively) are 1, or equivalently different from each other

```
module xorgate(A, B, F);  
  input A, B;  
  output F;  
  assign F = A ^ B;  
endmodule
```

Truth Table (XOR, XNOR)

A	B	$A \oplus B$	$\overline{A \oplus B}$
0	0	0	1
1	0	1	0
0	1	1	0
1	1	0	1

XNOR


- F is 1 when either A or B (exclusively) are 0, or equivalently equal

```
module xnorgate(A, B, F);  
  input A, B;  
  output F;  
  assign F = ~(A ^ B);  
endmodule
```

Implementation of Boolean Functions with Logic Gates

- Translate Boolean function into gate-level implementation
 - Logic gates as building blocks of any digital system
- Start simple: SOP form → gate-level design
 - Example of SOP with constraint: max number of logic gate inputs is 4 (fan-in)

 
$$F(w, x, y, z) = \bar{w}\bar{x}z + \bar{w}xz + wyz + xyz$$



if AND5 or more is needed: two-level ANDing (same for OR):

$$x_1 \cdot x_2 \cdot x_3 \cdot x_4 \cdot x_5 \cdot x_6 = (x_1 \cdot x_2 \cdot x_3 \cdot x_4) \cdot (x_5 \cdot x_6)$$

parentheses ($\sim w \& x \& z$) not needed in SOP, as precedence order is $\sim, \&, ^, |$

 


```
module func(w,x,y,z,F);  
  input w, x, y, z;  
  output F;  
  assign F = ~w & ~x & z | ~w & x & z | w & y & z | x & y & z;  
endmodule
```

Implementation of Boolean Functions with Logic Gates

- Another example of SOP with constraint: max number of logic gate inputs is 4
 
$$F(a, b, c, d) = ab\bar{c} + abc + bcd + \bar{a}cd + a\bar{b}\bar{c}d$$




```
module func(a,b,c,d,F);  
    input a, b, c, d;  
    output F;  
    assign F = a & b & ~c | a & b & c | b & c & d | ~a & c & d | a & ~b & ~c & d;  
endmodule
```


Implementation of Boolean Functions with Logic Gates

 - Example of POS with constraint: max number of logic gate inputs is 4

$$F(a, b, c) = (a + b + \bar{c})(a + c)(\bar{a} + \bar{b} + c)(a + \bar{b} + \bar{c})$$



parentheses needed in POS,
as precedence order is $\sim$, $\&$, $\wedge$, $|$

```
module func(a,b,c,F);  
  input a, b, c;  
  output F;  
  assign F = (a | b | ~c) & (a | c) & (~a | ~b | c) & (a | ~b | ~c);  
endmodule
```

Boolean Function Simplification

- To reduce the hardware cost, the Boolean function must be simplified before gate-level implementation
 - Eliminate redundancies, minimize gate count
- Definition of simplified Boolean Function
 - It contains a minimal number of **terms** and **literals** in each term, such that no other expression with fewer literals and terms will represent the original function

literals (variables, complemented or not)

$$F_2(A, B, C) = \bar{A}\bar{B}\bar{C} + A\bar{B} + \bar{B}C + AB\bar{C}$$

terms

literals

$$F_2(A, B, C) = (A + B + C) \cdot (A + \bar{B} + \bar{C})$$

terms


- Simplification can be carried out via
 - Algebraic manipulations using postulates and theorems
 - Karnaugh maps

Boolean Function Simplification using Algebraic Manipulations


- Example: SOP

$$\begin{aligned} F(a, b, c, d) &= \bar{a}\bar{b}\bar{c} + \bar{a}b\bar{c}\bar{d} + \bar{a}b\bar{c}d \\ &= \bar{a}\bar{b}\bar{c} + \bar{a}b\bar{c}(\bar{d} + d) \leftarrow (A + \bar{A} = 1) \\ &= \bar{a}\bar{c}(\bar{b} + b) \leftarrow (A + \bar{A} = 1) \\ &= \bar{a}\bar{c} \leftarrow (A + \bar{A} = 1) \end{aligned}$$

Before simplification

 

After simplification

 

Boolean Function Simplification using Algebraic Manipulations

- Another example: SOP


$$\begin{aligned}F(x, y, z) &= \bar{w}\bar{x}z + \bar{w}xz + xyz + wxy \\&= \bar{w}z(\bar{x} + x) + w(xy) + z(xy) \\&= \bar{w}z + w(xy) + z(xy) \\&= \bar{w}z + wxy\end{aligned}$$

$$\leftarrow (A + \bar{A} = 1)$$

$$\leftarrow (A + \bar{A} = 1)$$


$$\leftarrow (AB + \bar{A}C + BC = AB + \bar{A}C) - \text{consensus}$$

Before simplification

 

gate count = 7

After simplification

 

gate count = 4

(43% reduction!)

Boolean Function Simplification using Algebraic Manipulations

- Another example: SOP


$$\begin{aligned} F(a, b, c, d) &= ab\bar{c} + abc + bcd + \bar{a}cd + a\bar{b}\bar{c}d \\ &= ab(\bar{c} + c) + bcd + \bar{a}cd + a\bar{b}\bar{c}d \\ &= a[b + \bar{b}(\bar{c}d)] + bcd + \bar{a}cd \\ &= a(b + \bar{c}d) + bcd + \bar{a}cd \\ &= [ab + \bar{a}(cd) + b(cd)] + a\bar{c}d \\ &= ab + \bar{a}cd + a\bar{c}d \end{aligned}$$

$$\leftarrow (A + \bar{A} = 1)$$

$$\leftarrow (A + \bar{A} \cdot B = A + B)$$


$$\leftarrow (AB + \bar{A}C + BC = AB + \bar{A}C) - \text{consensus}$$

Before simplification

 

gate count = 11

After simplification

 

gate count = 6

(45.5% reduction!)

Boolean Function Simplification using Algebraic Manipulations

- Disadvantage of algebraic manipulations: not systematic, tedious, no guarantee of minimal function
- Proposed procedure to somewhat minimize Boolean functions using algebraic manipulations

$$1) AB + A\bar{B} = A \quad (\text{Logical adjacency})$$

$$2) A + \bar{A} \cdot B = A + B$$

$$3) AB + \bar{A}C + BC = AB + \bar{A}C \quad (\text{Consensus})$$

- Apply (1) until it cannot be applied further
- Apply (2) until it cannot be applied further
- Go back to (1) and then (2) until they can no longer be applied
- Apply (3) until it cannot be applied further
- Go back to (1), (2) and then (3) until none of them can be applied

Interfaces and Legacy Systems: Negative Logic

- Physical logic gates: voltage input and output levels low (L) and high (H)


- Binary values 0 and 1 can be mapped in two ways

- positive logic ("active high"): ex. X.H
- negative logic ("active low"): ex. X.L
- convert one to another via simple inverter

voltage level	positive logic value (X.H)	negative logic value (X.L)
H	1	0
L	0	1




- In the (distant) past, active-low preferred because of lower power in H level

 - normally-off signals (e.g., reset) were set to H (e.g., TTL logic, open-collector)
- it was easier to merge normally-off signals into one occasionally-on signal
- today used only in system resets, interrupts and I²C busses



- Today (including FPGAs), no preference

   - think in terms of positive logic, negate any active-low input/output signal if necessary
- graphically add "bubble" to signals to remind about the complement



Bubble Pushing Rule

- Graphical interpretation of De Morgan's law(s), useful to
 - Manipulate gate-level netlists directly without Boolean expressions (tedious)
 - Transform logic gates from one type (e.g., NAND) into another one (NOR)
- Graphically, bubble = complement
 - If a bubble is needed, it can always be created anywhere (but in pairs)
 - Vice versa, two adjacent bubbles can always be dissolved

$$\text{---} \xrightarrow{\text{red arrow}} \text{---} \circ \text{---} \quad \bar{\bar{A}} = A$$


$$\text{---} \circ \text{---} \xrightarrow{\text{red arrow}} \text{---} \quad A = \bar{\bar{A}}$$

- Bubbles at input of AND gate can be “pushed” at its output, and the gate is transformed into a NOR gate (similarly, NAND becomes OR)



$$\bar{A} \cdot \bar{B} = \overline{A + B}$$



 and vice versa
(push from
output to input)


  
$$\bar{A} + \bar{B} = \overline{A \cdot B}$$




Bubble Pushing Rule

- Example: implement Boolean function using only NOR gates and inverter gates


$$F = \overline{(\overline{A} \cdot B + \overline{A} \cdot C)}$$

Step 1: place logic gates

 


Step 3: bubble pushing

 - Replace gates with targeted ones
- balance the bubbles using inverters to maintain the correct functionality




Step 2: add bubbles and connect

 (add the complement where needed for the correct function)



Step 4: simplify

(eliminate redundant pairs of bubbles)

 

A	B	$\overline{A} \cdot B$
0	0	1
1	1	0

A	B	$\overline{A + B}$
0	0	1
1	1	0

Bubble Pushing Rule

- Another example: implement Boolean function with logic gates with active-low output, using only NAND gates (no inverter gates)

In Summary

- Logic gates
 - Building blocks of any digital system
 - Different levels of abstraction (Boolean, truth table, graphical, Verilog)
- Implementation of Boolean function using gates
- Design simplification via algebraic manipulations (limitations motivate introduction of K-maps)
- Positive $\rightarrow$ negative logic conversion for legacy systems
- Bubble pushing for direct manipulation of gate-level netlists (with no intermediate Boolean manipulations)